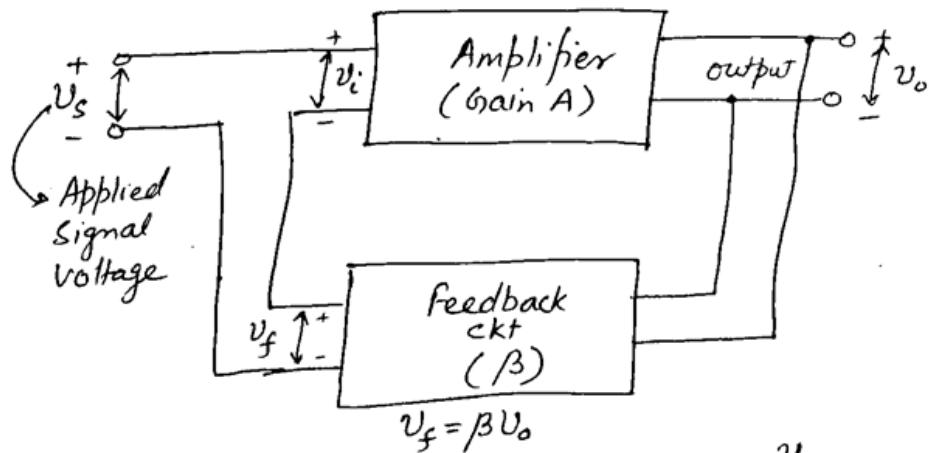


FEEDBACK IN AMPLIFIERS[4 Lectures]

⇒ An Amplifier circuit amplifies (increases) Signal strength (Not only information but also noise)

Principle of Feedback in Amplifier

$$A = \text{Gain of the Amplifier ckt} = \frac{V_o}{V_i}$$

⇒ Feedback network provides a fraction of output as the feedback voltage to the input section of Amplifier ckt
so $V_f = \beta V_o$, $\beta < 1$ (Called "Feedback Ratio/Fraction")

Positive Feedback: $V_i = V_s + V_f = V_s + \beta V_o$

Negative Feedback: $V_i = V_s - V_f = V_s - \beta V_o$

How Gain (A) is affected in feedback?

Negative Feedback: The gain is given as the ratio of output voltage (v_o) to the input volt (v_i)

$$\text{So } A_{\text{neg}} = \frac{v_o}{v_i} = \frac{v_o}{(v_s - \beta v_o)}$$

$$\Rightarrow A_{\text{neg}} (v_s - \beta v_o) = v_o$$

$$\Rightarrow A_{\text{neg}} v_s = v_o (1 + \beta A)$$

$$\Rightarrow \boxed{\frac{v_o}{v_s} = \frac{A}{(1 + \beta A)}} = A_{\text{fn}} \quad \begin{matrix} \text{(overall gain} \\ \text{with the Negative} \\ \text{Feedback of Amplifier)} \end{matrix}$$

$$\text{So } A_{\text{fn}} = \frac{\text{Gain with Negative Feedback}}{(1 + \beta A)} = \frac{A}{(1 + \beta A)} \quad \& \quad \boxed{A_{\text{fn}} < A} \\ \because (1 + \beta A) > 1$$

★ \Rightarrow So Negative Feedback reduces/decreases the Gain of the Amplifier ckt.

Positive Feedback: Again $A = \frac{v_o}{v_i} = \frac{v_o}{(v_s + \beta v_o)}$

$$\Rightarrow A(v_s + \beta v_o) = v_o \Rightarrow A v_s = v_o (1 - \beta A)$$


$$\Rightarrow \boxed{\frac{v_o}{v_s} = \frac{A}{(1 - \beta A)}} = \frac{\text{Gain with Positive Feedback}}{(1 - \beta A)}$$

$$\text{Since } (1 - \beta A) < 1 \quad \text{so } \Rightarrow \boxed{A_{\text{fp}} > A}$$

i.e. $\star \Rightarrow$ Positive feedback Increases the Gain of the Amplifier ckt.

Advantages/Disadvantages of Feedback

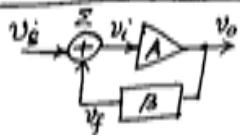
Positive Feedback: In this case the feedback, i.e. the



part of output signal (voltage or current), is in phase (180°) with the input signal and hence enhances/increases it.

- It "Increases" the Gain (A_{fp}) of the Amplifier.
- However, it also increases Distortion (Noise) in ckt.
- Increases Instability in the ckt.
- Used in 'Oscillator Circuits'.
- It is also called 'Regenerative Feedback'.

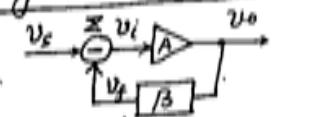Negative Feedback: In this case the feedback part (voltage/current) is out of Phase (180° difference) with input signal & hence reduces/decreases it.



- It "Decreases" the Gain (A_{fn}) of the Amplifier, but Gain is Stabilized
- But "Distortion" is Reduced (all types of feedback) (Harmonic or Nonlinear) in Distortion
- "Noise" is Reduced
- Input Impedance/Resistance Changes] as given below in Table.
- Output Impedance/Resistance Changes] as given below in Table.
- Operating Point is Stabilized.
- Used in a wide range of applications :
 - Amplifiers, Regulated Power Supply etc.
- It is also called 'Degenerative Feedback'.

Bandwidth is increased/extended in all 4 types of feedback (negative) feedback

Volt. Series	Current Series	Volt. Shunt	Current Shunt
$R_{if} \uparrow R_i(1+P_{if}) \uparrow$	$R_o(1+P_{if}) \uparrow$	$\frac{R_i}{(1+P_{if})} \downarrow$	$\frac{R_o}{(1+P_{if})} \downarrow$

Volt. Series	Current Series	Volt. Shunt	Current Shunt
$R_{if} \downarrow R_i(1+P_{if}) \downarrow$	$R_o(1+P_{if}) \uparrow$	$\frac{R_i}{(1+P_{if})} \downarrow$	$\frac{R_o}{(1+P_{if})} \downarrow$