

- Sinusoidal Oscillators:
- Output waveform is a SINE wave
  - Also called 'Harmonic Oscillators'
  - Output freq.s 20Hz - 1GHz
- Non-sinusoidal Oscillators:
- Output waveform is Square, Triangular, Sawtooth etc.
  - Also called 'Relaxation Oscillators'
  - Output freq.s - upto 20MHz.

Sinusoidal Oscillators


- Tuned Circuit Oscillators (LC Tankckt)
  - called R.F. (Radio freq.) Oscillators
  - Hartley, Colpitt etc.
- RC Oscillators
  - Audio freq. Osc.s
  - Phase Shift & Wein-Bridge
- Crystal Oscillators
  - used Quartz Crystals
- Negative-Resistance Osc.
  - use tunnel devices

BARKHAUSEN Criterion for Self-Sustained Oscillations

- Feedback must be "POSITIVE" (Phase shift of  $0^\circ/360^\circ$ )
- Loop Gain ( $= A\beta$ ) must be  $\geq 1$
- $\Rightarrow A\beta > 1$  initially for starting Oscillations  $\rightarrow$  By either reducing  $A$  or  $\beta$
- $\Rightarrow A\beta = 1$  Afterward for sustaining Oscillations.

$A\beta = 1 \angle 0^\circ \text{ or } 360^\circ$

$\beta =$  Feedback Fraction

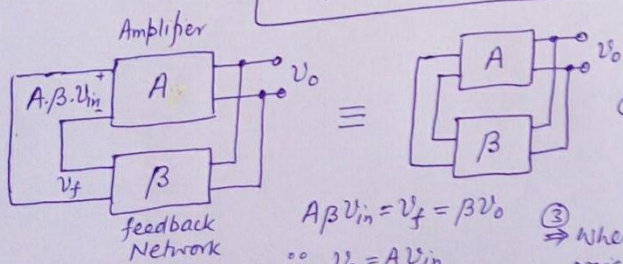

- ①  $\Rightarrow$  Starting Voltage is "THERMAL NOISE"
- ②  $\Rightarrow$  Random movement of free electrons in a resistor generates a Noise voltage across that resistor.
- ③  $\Rightarrow$  When power is first turned ON, these noise voltages gets amplified & appear at the output. - It contains all frequencies upto 1000 GHz.

- ④  $\Rightarrow$  Above & Below Resonant frequency Phase shift  $\neq 0^\circ \text{ or } 360^\circ$
- ⑤  $\Rightarrow$  Hence Oscillations are sustained only at the Resonant frequency of the feedback Network.



## Advantages/Disadvantages of LC & RC Networks in Oscillator Circuits

- Frequencies  $< 1\text{ MHz}$  : RC Oscillators are used to produce almost perfect sine waves (Op-Amps + BJT are suitable)
- Frequencies  $> 1\text{ MHz}$  : LC Resonant circuits are used (BJT + FET are used (Op-Amp Not suitable))

Disadvantages of LC circuits :

- Frequency instability
- Unsuitable for low frequencies
- Inductors (Bulky, Expensive)
- Waveform quality not good.

Advantages of LC Circuits :

- Can produce High Freq. Oscillations (1-500 MHz)

Advantages of RC Network :

- All drawbacks of LC Osc. ckt's are eliminated
- Less bulky & expensive
- Can produce low frequencies
- Waveform stability is very good & output is distortion free


— Commonly used for generating Audio frequencies.

Disadvantages of RC Network :

- Due to small feedback, starting oscillations becomes difficult.
- Output signal is small.
- To increase feedback, High value of  $V_{cc}$  is required.



# RC PHASE SHIFT OSCILLATOR

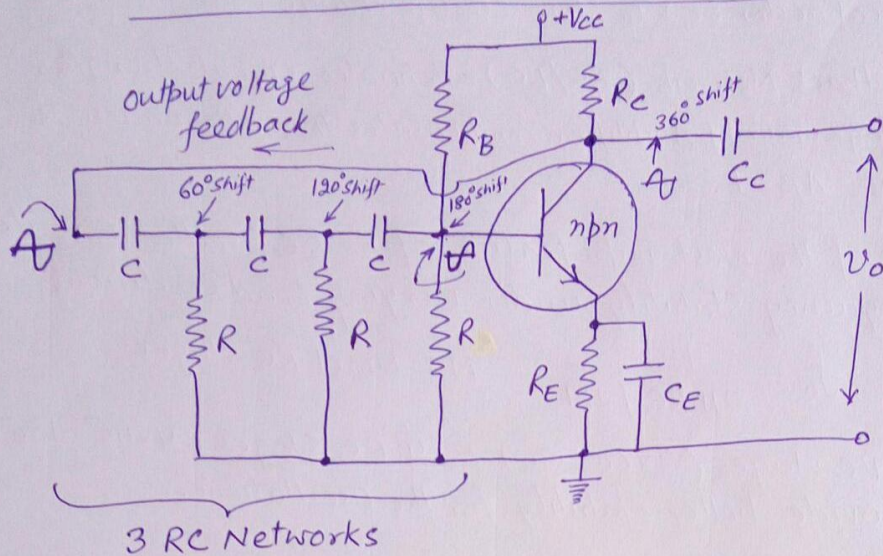

- This type of Oscillator uses an Amplifier Configuration in combination with 3 RC-Networks.
- Each RC Network produces a  $60^\circ$  phase shift between the input and output signal. So 3 RC networks produce a combined phase shift of  $180^\circ$ .
- A further  $180^\circ$  phase shift is produced by the Amplifier configuration, resulting in a total  $360^\circ$  phase shift or "Positive Feedback".
- with sufficient biasing & hence adequate amplification Sustained Oscillations can be maintained.

RC Phase Angle: Since  $X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$

Total Impedance of a Single RC Network is

$$Z = \sqrt{R^2 + X_C^2} \quad \text{and} \quad \phi = \tan^{-1}\left(\frac{X_C}{R}\right)$$

⇒ Properly chosen  $X_C$  (i.e. value of  $C$ ) and  $R$  can make  $\phi = 60^\circ$

⇒ Frequency of Oscillations:  $f_0 = \frac{1}{2\pi\sqrt{6}(RC)}$

Feedback Fraction:  $|\beta| = \frac{1}{29}$  so  $(A_v)_{\min} = 29$  } Applicable for FET Amplifier Configuration

⊛ For a Transistor (small signal CE Config) Short circuit Current Gain  $h_{fe}$  should be equal to or more than 44.5 for sustained Oscillations.

$h_{fe} > \frac{29}{k} + 4k + 23 \Rightarrow (h_{fe})_{\min} = 44.5$  for  $k = 2.7 \Rightarrow \beta = -\frac{1}{20} \Rightarrow |A| = \left|\frac{1}{\beta}\right| = 20$  for BJT config.