

Course: B.Sc (Hons) PHYSICS

PAPER : Analog Systems & Applications
(Code: 32221403)

Semester: IV Section: A

Name of Teacher : Dr. V.K. Paliwal

Types of Negative Feedback

Two main types:
 -> Negative Voltage feedback
 -> Negative Current feedback

Negative Voltage feedback
 -> Voltage-Series feedback
 -> Voltage-Shunt feedback


Negative Current feedback
 -> Current-Series feedback
 -> Current-Shunt feedback

Total 4 types of Neg feedback

① Voltage-Series feedback:


$V_f = \beta V_o$

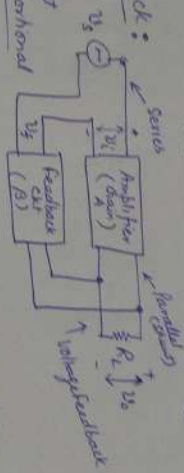② Voltage feedback to the input section of amplifier is proportional to the output voltage (V_o).
 => A fraction of output voltage ($= \beta V_o$) is applied in series with input voltage V_s .




③ Voltage-Shunt feedback:

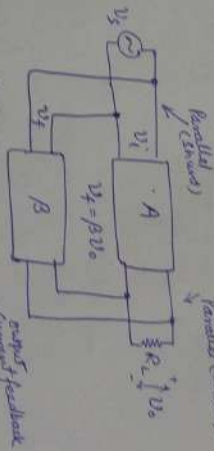=> Now a fraction of output voltage ($= \beta V_o$) is applied in parallel (shunt) with input voltage V_s .




④ Current-Series feedback:

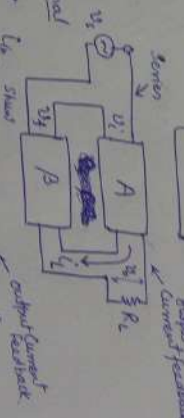② Voltage feedback to the input section of amplifier is proportional to the output current (I_o).
 => voltage feedback is applied in series to input




④ Current-Shunt feedback:

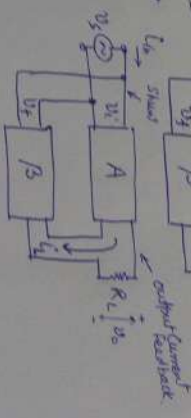=> Voltage feedback is applied parallel to the input voltage



Advantages/Disadvantages of Feedback


Positive Feedback:

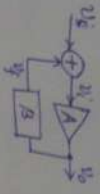

In this case the feedback, i.e. the part of output signal (voltage or current), is in phase with the input signal and hence enhances/increases it.

- It increases the Gain (A_{fb}) of the Amplifier.
- However, it also increases Distortion (Noise) in it.
- Increases Instability in the circuit.
- Used in 'Oscillator Circuits'.
- It is also called 'Regenerative Feedback'.

Negative Feedback:

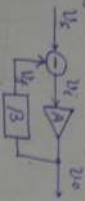

In this case the feedback part (voltage/current) is out of phase (180° difference) with input signal & hence reduces/decreases it.

- It 'Decreases' the Gain (A_{fb}) of the Amplifier, but Gain is Stabilized.
- But 'Distortion' is Reduced. (Harmonic or Non-linear Distortion)
- 'Noise' is Reduced.
- Input Impedance/Resistance is Increased.
- Output Impedance/Resistance is Decreased.
- Operating Point is Stabilized.
- Used in a wide range of applications:
 - Amplifiers, Regulated Power Supply etc.
- It is also called 'Degenerative Feedback'.

How Gain (A) is affected in feedback?

(A) without feedback

Negative feedback: The gain is given as the

ratio of output voltage (V_o) to the input volt (V_i)

$$A_{\text{neg}} = \frac{V_o}{V_i} = \frac{V_o}{(V_i - \beta V_o)}$$

$$\Rightarrow A_{\text{neg}} (V_i - \beta V_o) = V_o$$

$$\Rightarrow A_{\text{neg}} V_i = V_o (1 + \beta A)$$

$$\Rightarrow \boxed{\frac{V_o}{V_i} = \frac{A}{(1 + \beta A)}} = A_{\text{fn}} \quad \begin{matrix} \text{Overall gain} \\ \text{with the} \\ \text{Negative} \\ \text{Feedback of Amplifier} \end{matrix}$$

So $A_{\text{fn}} = \text{Gain with Negative Feedback} = \frac{A}{(1 + \beta A)}$ & $A_{\text{fn}} < A$
∴ $(1 + \beta A) > 1$

⊛ So Negative feedback reduces/decreases the Gain of the Amplifier ckt.

Positive feedback: Again $A = \frac{V_o}{V_i} = \frac{V_o}{(V_i + \beta V_o)}$

$$\Rightarrow A (V_i + \beta V_o) = V_o \Rightarrow A V_i = V_o (1 - \beta A)$$

$$\Rightarrow \boxed{\frac{V_o}{V_i} = \frac{A}{(1 - \beta A)}} = A_{\text{fp}} = \text{Gain with Positive Feedback}$$

Since $(1 - \beta A) < 1$ so \Rightarrow ~~$A_{\text{fp}} < A$~~ $A_{\text{fp}} > A$

⊛ i.e. \Rightarrow Positive feedback Increases the Gain of the Amplifier ckt.

Date: 16.03.2020


UNIT 5

FEEDBACK IN AMPLIFIERS

[4 Lectures]

⇒ An Amplifier circuit amplifies (increases) signal strength (Not only information but also noise)

Principle of feedback in Amplifier

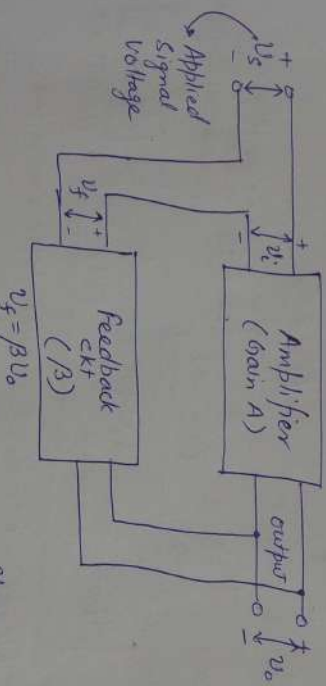

$$A = \text{Gain of the Amplifier ckt} = \frac{V_o}{V_i}$$

⇒ Feedback network provides a fraction of output as the feedback voltage to the input section of Amplifier ckt
So $V_f = \beta V_o$, $\beta < 1$ (called 'feedback ratio/fraction')

Positive Feedback:

$$V_i = V_s + V_f = V_s + \beta V_o$$

Negative Feedback:

$$V_i = V_s - V_f = V_s - \beta V_o$$