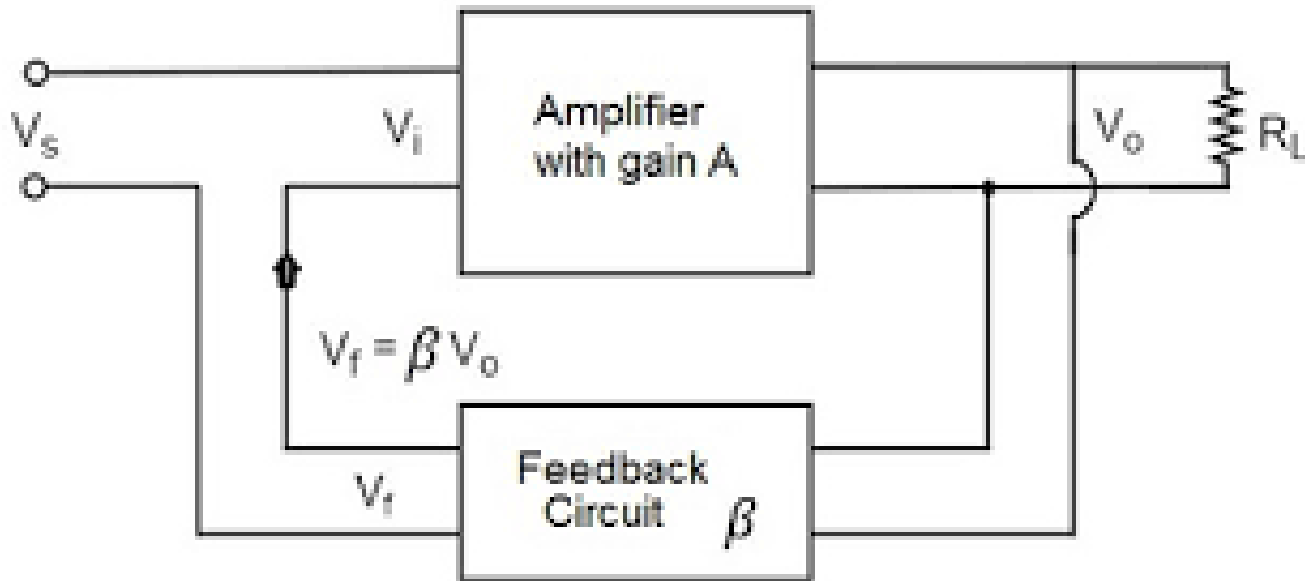


Effects of Negative Feedback on Amplifier Parameters

Applicable for Voltage Amplifier with Voltage Series Feedback



- Input Impedance is Increased

$$R_{i(\text{feedback})} = R_i(1 + \beta A)$$

- Output Impedance is Decreased

$$R_{o(\text{feedback})} = \frac{R_o}{(1 + \beta A)}$$

- Voltage Gain with Neg.Feedback (A_F)
Decreases

$$A_{\text{Feedback}} = \frac{A}{(1 + \beta A)}$$


- **Bandwidth is Increased (B.W. = $f_{high} - f_{low}$)**

- **Higher cut-off frequency is Increased with Neg. Feedback**

$$f_{high(Feedback)} = f_{high} (1 + \beta A)$$

- **Lower cut-off frequency is Decreased with Neg. Feedback**
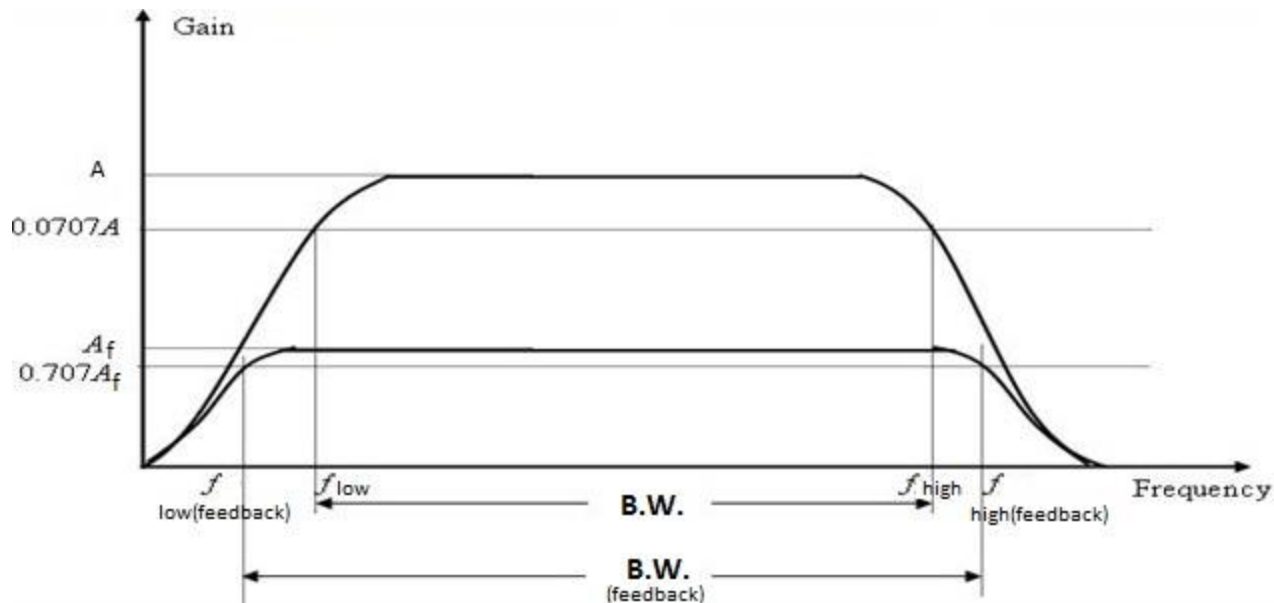
$$f_{low(Feedback)} = \frac{f_{low}}{(1 + \beta A)}$$



- **Gain Sensitivity is Reduced**

$$\left| \frac{dA_F}{A_F} \right| = \frac{1}{|1 + \beta A|} \left| \frac{dA}{A} \right|$$

- If Amplifier has 20dB of Neg. Feedback *i.e.* $[(1 + \beta A) = 10]$

- **So, if** $\left| \frac{dA}{A} \right| = 10\%$

- (i.e if there is 10% change in differential Volt.Gain without Feedback)

- **Then we have** $\left| \frac{dA_F}{A_F} \right| = 1\%$

(only 1% change in differential Volt.Gain with Neg. Feedback)

•Reduction in Non-Linear Distortion (NLD)

- NLD occurs with large input signals and produces harmonics of the input signal
- Negative Feedback reduces Total Harmonic Distortion (THD)

$$(THD)_F = \frac{THD}{(1 + \beta A)}$$

•So, if $|\beta A| \gg 1$ Then $(THD)_F \ll THD$

•Stability of Gain (A_F) is Improved

-So, if $|\beta A| \gg 1$ Then $A_F \approx 1/\beta$

- So, Closed-loop Gain (A_F) can be made insensitive (independent) of Open loop Gain (A)

•Noise is Reduced & Signal-to-Noise Ratio is Improved