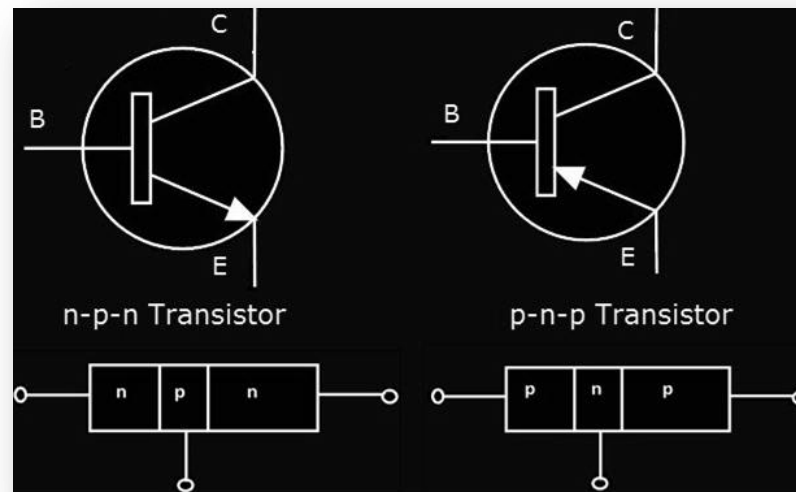


UNIT 3

Bipolar Junction Transistor

What is Bipolar Junction Transistor (BJT)

- Bipolar Junction means:
 - 2 PN Junctions: Current goes through 2 types of Semiconductor material P & N
 - Uses both “Electrons” & “Holes” as Charge Carriers (Bipolar: 2 polarities),
:although holes mobility is much less than that of electrons
- Two types of BJT are :- NPN & PNP
 - B: Base, C: Collector, E: Emitter





Types of BJT Configurations


- 3 – Types: CB, CE, CC
 - CB: Common-Base
 - CE: Common-Emitter
 - CC: Common-Collector

- Common Term (Base/Emitter/Collector) implies that, *the Term (Base/Emitter/Collector) is common to both Input and Output Circuits/Sections of the above 3 BJT Configurations.*

Common-Base (CB) Configuration

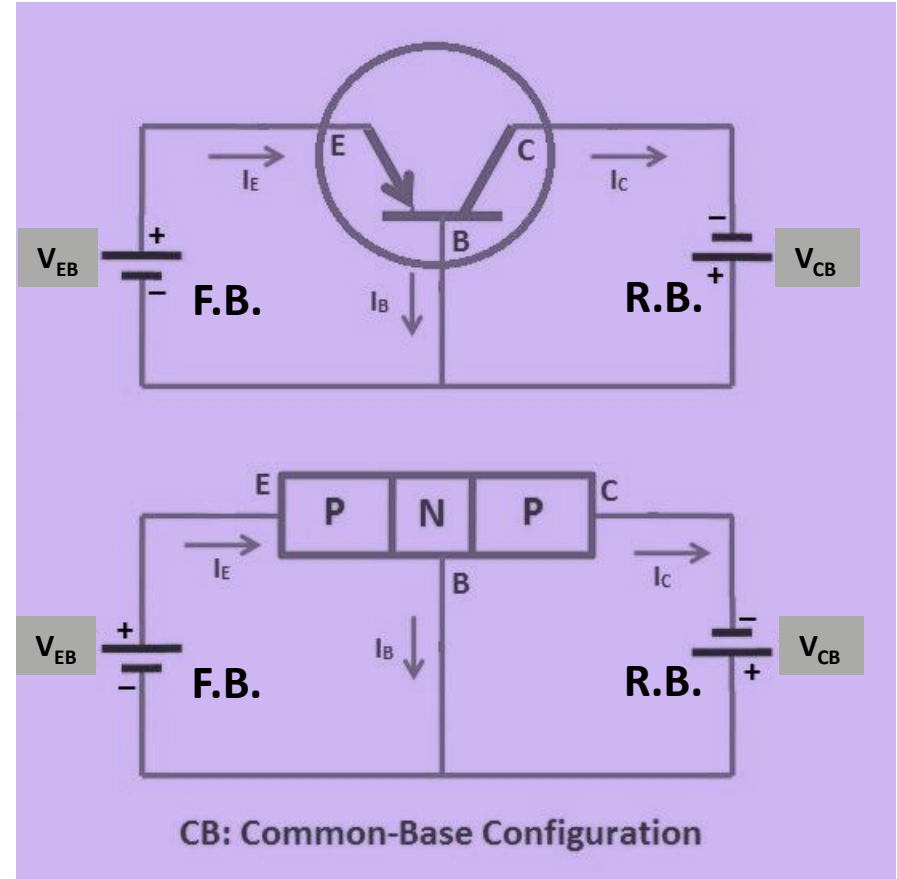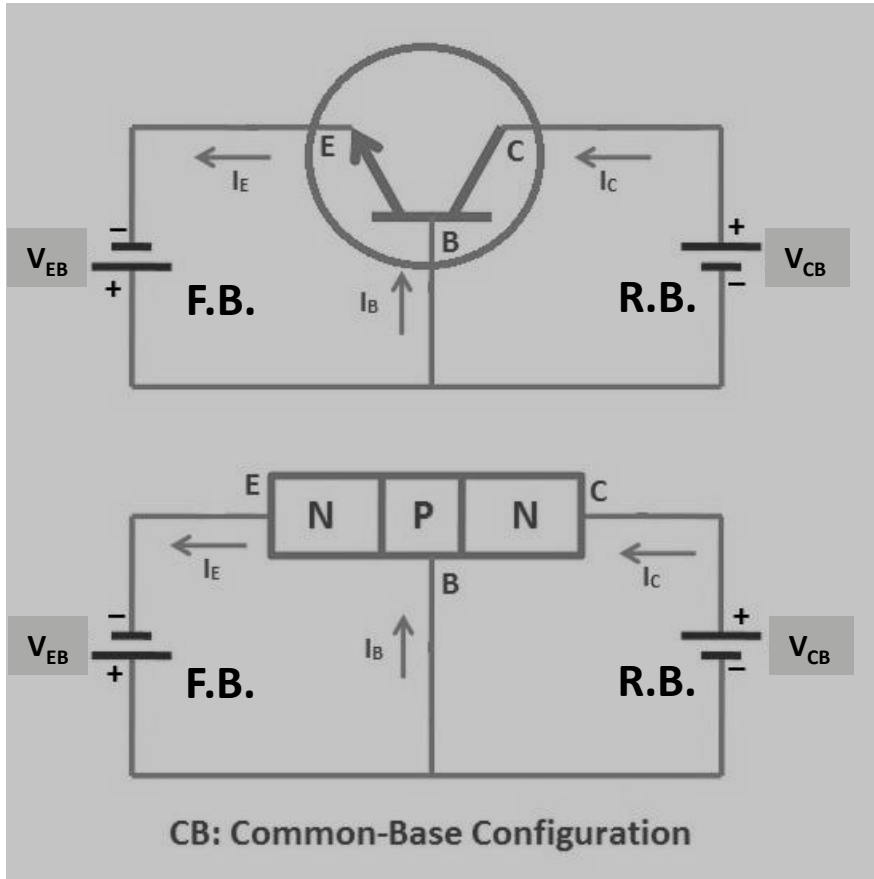

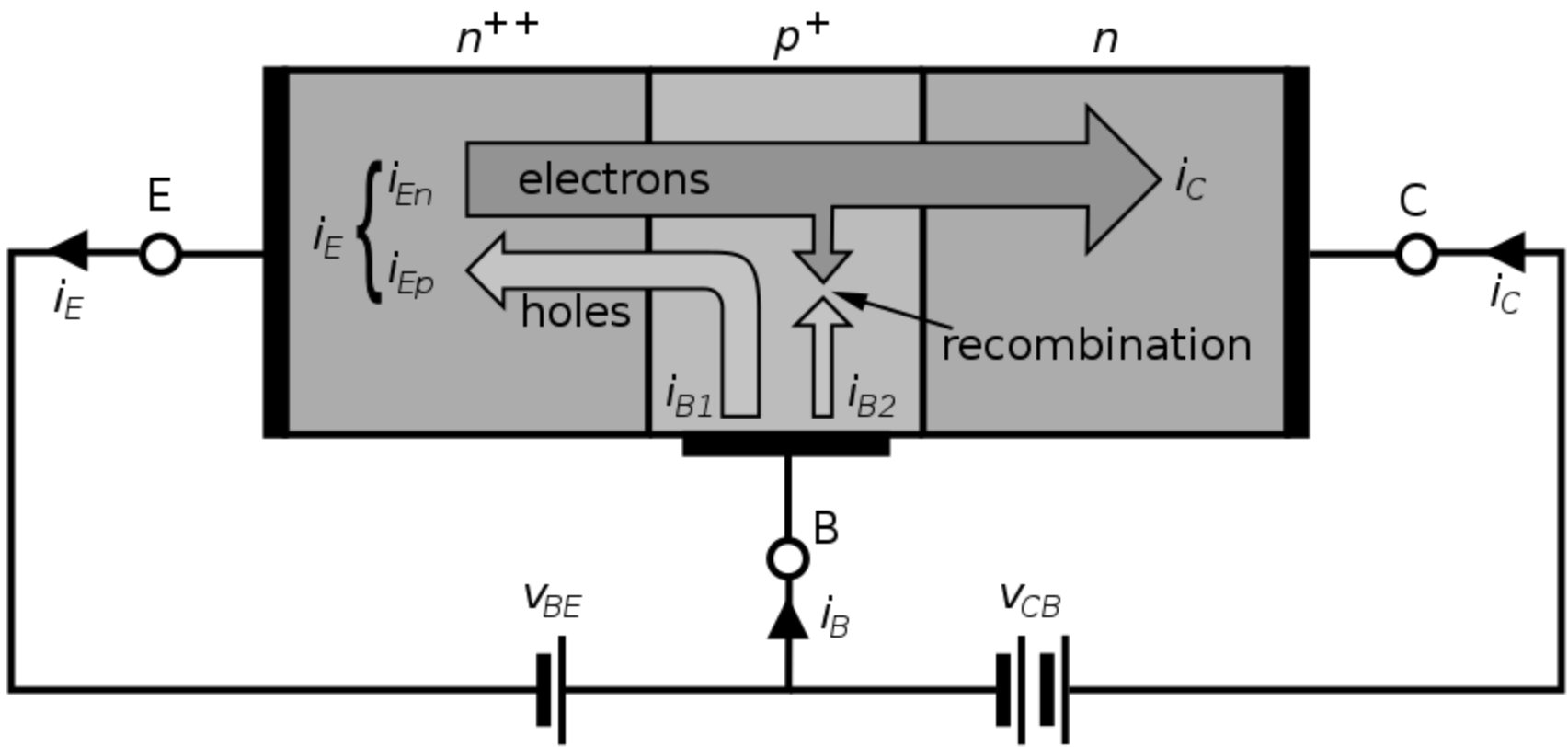- NPN and PNP – CB Configurations have different voltage arrangements, such that
 - Input Section is always Forward Biased (F.B.) &
 - Output Section is always Reverse Biased (R.B.)




Source: https://en.wikipedia.org/wiki/Bipolar_junction_transistor

Current-Voltage (I-V) Characteristics of npn – CB configuration

- **Input (or Emitter) Static Characteristics:**

- **Input Current (I_E) vs Input Voltage (V_{EB})**

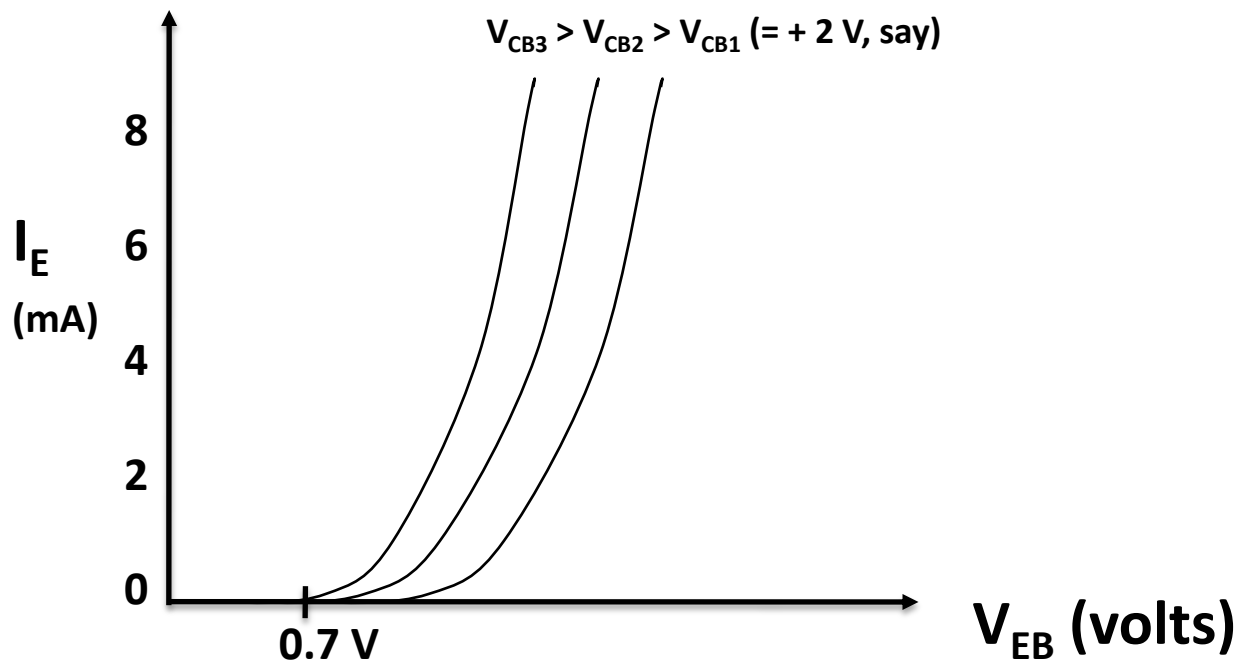- @ Constant value of Collector-Base Voltage (V_{CB}) for each curve




Current-Voltage (I-V) Characteristics of npn – CB configuration

- **Output (or Collector) Static Characteristics:**

- Output Current (I_C) vs Output Voltage (V_{CB})


- @ Constant value of Emitter Current (I_E) for each curve

$$I_E = I_C + I_B$$
$$\approx I_C$$

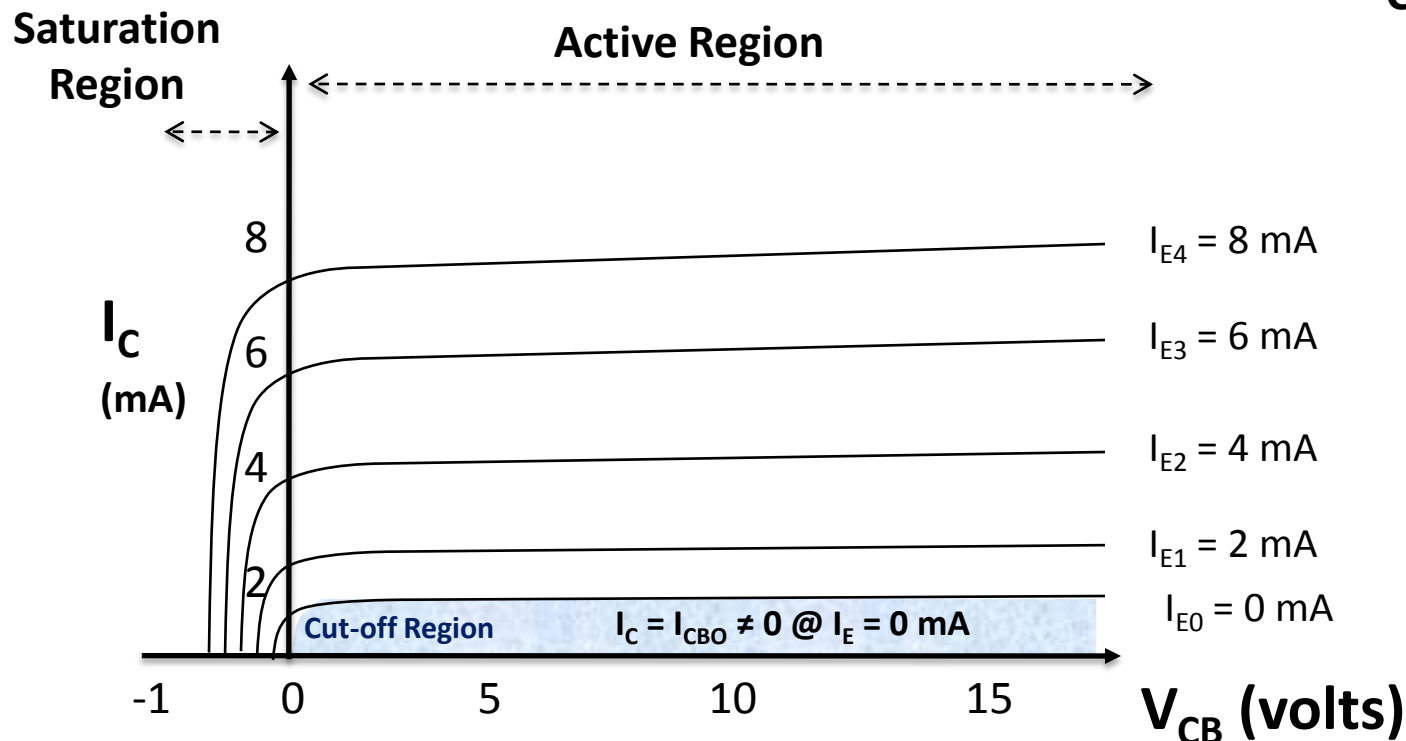

Input (or Emitter) Static Characteristics

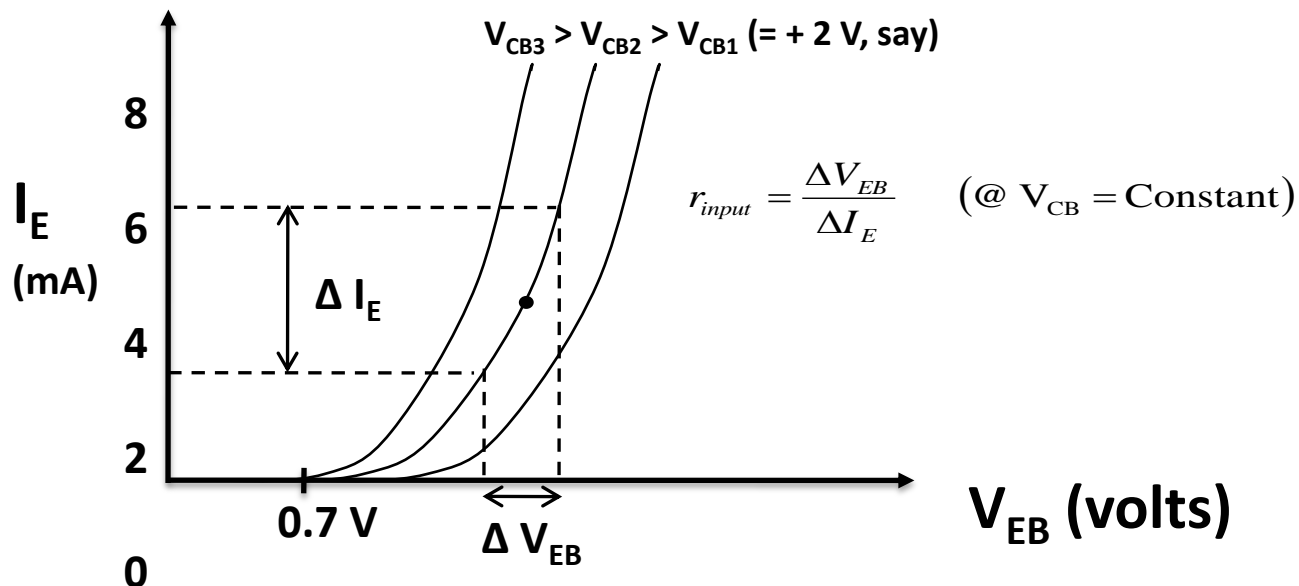- Represents simply the Forward Characteristics of Emitter-Base Diode (@ various Collector Voltages)
- Threshold Voltage below which I_E is Very Small
 - 0.6-0.7 V (Si) and 0.1 V (Ge) materials
- Input Curves will shift towards left as V_{CB} Increases.



- Dynamic Input Resistance (r_i) can be calculated from I/P characteristics
- It varies with the point of measurement
- Typical values of r_i are $\approx 20 - 100 \Omega$
- So, Input Resistance of CB config. is Very Low

Output (or Collector) Static Characteristics

- Divided into 3 Regions: - Active Region, - Saturation Region, - Cutoff Region

	Active Region	Saturation Region	Cutoff Region
Emitter-Base	<i>Forward Biased</i>	Forward Biased	Reverse Biased
Collector-Base	<i>Reverse Biased</i>	Forward Biased	Reverse Biased

Active Region:

- I_C is essentially independent of V_{CB}
- I_C depends only upon I_E
- Curves are nearly flat in Active region

- For $I_E = 0$, $I_C = I_{CBO}$ (or I_{CO}) $\neq 0$ [called "Reverse Saturation/Leakage Current"]
- "Reverse Saturation/Leakage Current (I_{CO}) - μA for Ge, nA for Si

$$I_C = I_E - I_B$$

&

$$I_C = \alpha_{dc} I_E + I_{CO}$$

Output (or Collector) Static Characteristics

$$\alpha_{dc} = \frac{I_C - I_{CO}}{I_E} \approx \frac{I_C}{I_E} \quad \text{as } I_{CO} \ll I_C$$

α_{dc} is called “Large Signal Current Gain” or simply “dc alpha”


= Fraction of total emitter current (i.e. electrons) that have traveled from emitter across base to the collector region.

- Typical value of $\alpha_{dc} \approx 0.98$ (usually range between 0.90 – 0.995)
- It is not a constant but varies with I_E , V_{CB} & Temperature.

$$\alpha \text{ (or } h_{fb} \text{)} = \frac{\Delta I_C}{\Delta I_E} \quad (\text{@ constant } V_{CB})$$

α is called “Small Signal Short circuit Current Transfer Ratio or Gain” or simply “ac alpha”

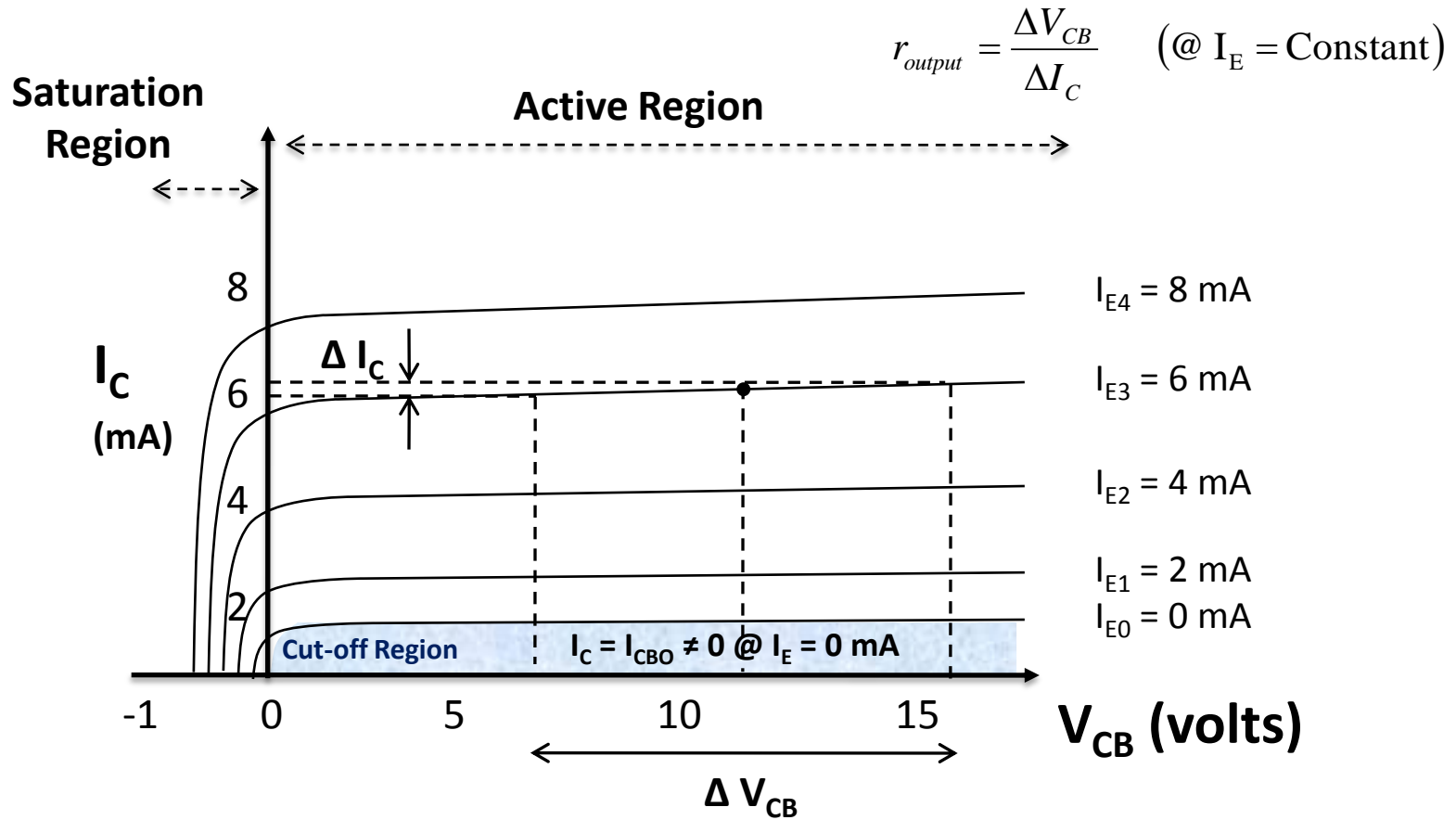Output (or Collector) Static Characteristics



- Dynamic Output Resistance (r_o) can be calculated from O/P characteristics
- It does not vary much as curves are almost flat (slope doesn't change much)
- Typical values of r_o are $\approx 1 \text{ M } \Omega$
- So, Output Resistance of CB config. is Very Very Large

Output (or Collector) Static Characteristics

Saturation Region:

- Both E-B and C-B Junctions are Forward –Biased
- As V_{CB} becomes Negative (for npn), the C-B Junction becomes Forward Biased
- Due to C-B_{Forward-Bias}, I_C changes are large for very small change in V_{CB} (Negative values)
- I_C , therefore, sharply decreases (for a given I_E)
- In Saturation Region, I_C doesn't depend much on I_E

Cutoff Region:

- As both E-B and C-B Junctions are Reverse –Biased
- Only Reverse Leakage/Saturation Current I_{CO} (or I_{CBO}) flows in the output circuit